

---

---

---

---

---

---

---

---

- The current is the same everywhere in a simple electric circuit.
- The voltage drops as you go through a resistor (or component).
  - Energy is used by the resistor (or component).
- The voltage drop across the resistor can be calculated with Ohm's law.

$$V_{resistor} = IR$$

---

---

---


---

---

---

---

---

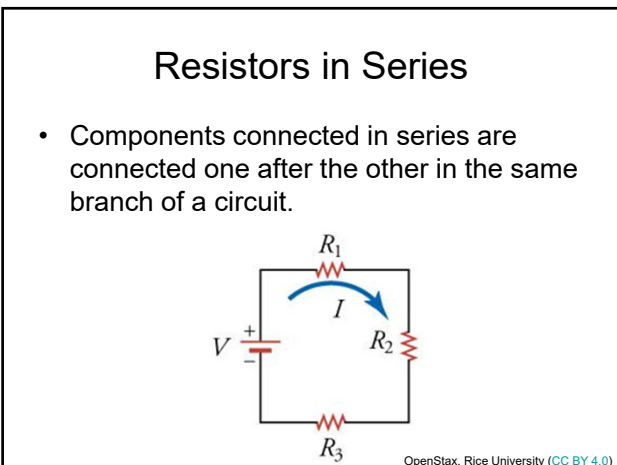

OpenStax, Rice University (CC BY 4.0)

---

---

---

---


---

---

---

---

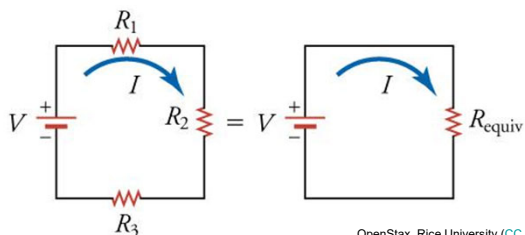- We can calculate an equivalent resistance to the resistors in this circuit.
  - An equivalent resistor is a resistor that has the same resistance as the combined resistance of a set of other resistors.
  - $V_{battery} = IR_{equiv}$



OpenStax, Rice University (CC BY 4.0)

---

---

---

---

---

---

---

---

- In a series circuit, the same current flows through all the components.
  - There is only one path.
- The voltage drop across each resistor is  $V = IR$ .
- The sum of these voltages must equal the output of the battery.

$$V_{battery} = V_1 + V_2 + V_3$$

$$V_{battery} = IR_1 + IR_2 + IR_3$$

---

---

---

---

---

---

---

---

$$V_{battery} = I(R_1 + R_2 + R_3)$$

$$\frac{V_{battery}}{I} = R_1 + R_2 + R_3$$

but  $R_{equiv} = \frac{V_{battery}}{I}$

so

$$R_{equiv} = R_1 + R_2 + R_3$$

---

---

---

---

---

---

---

---

- A circuit with resistors in series is known as a **voltage divider**.
- The voltage is divided among the resistors.

---



---



---



---



---




---



---
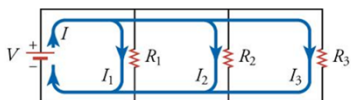
## Resistors in Parallel

- Components are in parallel when both ends of each component are connected directly together.
- There are multiple ways for the current to travel.



OpenStax, Rice University (CC BY 4.0)

---



---



---



---



---



---



---

- In a parallel circuit, the voltage drop across each component is the same.
  - They are connected (to the same wire) on both sides of the component.
- The current through each component may be different as the resistance may be different.
- The voltage across each resistor is
 
$$V = I_1 R_1 = I_2 R_2 = I_3 R_3$$
- Rearranging these equations gives

$$I_1 = \frac{V}{R_1} \quad I_2 = \frac{V}{R_2} \quad I_3 = \frac{V}{R_3}$$

---



---



---



---



---



---



---

- Charge is conserved. Therefore, the sum of the individual currents is the total current in the circuit,  $I$ .

$$I = I_1 + I_2 + I_3$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\frac{I}{V} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

---

---

---

---

---

---

---

---

but

$$\frac{1}{R_{equiv}} = \frac{I}{V}$$

so

$$\frac{1}{R_{equiv}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

---

---

---

---

---

---

---

---

- A circuit with resistors in parallel is known as a **current divider**.
  - The current is divided among the resistors.

---

---

---

---


---

---

---

---

## Example

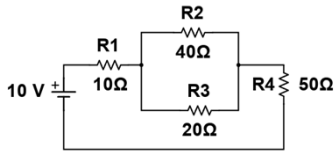

Calculate the equivalent resistance of the circuit, the voltage drop across each resistor, and the current through each resistor.

---

---

---

---

---

---

---

---

R2 and R3 are in parallel.

$$\frac{1}{R_{EQ1}} = \frac{1}{40} + \frac{1}{20}$$

$$R_{EQ1} = 13.33\Omega$$

R1, REQ1, and R4 are in series.

$$R_{EQ2} = 10 + 13.33 + 50$$

$$R_{EQ2} = 73.33\Omega$$


---

---

---

---

---

---

---

---


$$I = \frac{V}{R} = \frac{10}{73.33} = 0.136 \text{ A}$$

R1, REQ1, and R4 are in series.  
Therefore, all have the same current.

$$I_{R1} = I_{REQ1} = I_{R4} = 0.136 \text{ A}$$

$$V_{R1} = (0.136)(10) = 1.36 \text{ V}$$

$$V_{REQ1} = (0.136)(13.33) = 1.81 \text{ V}$$

$$V_{R4} = (0.136)(50) = 6.8 \text{ V}$$


---

---

---


---

---

---

---

---

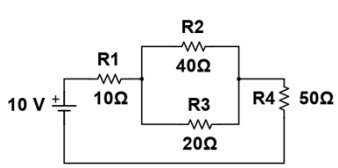

R2 and R3 are in parallel. Therefore, the voltage drop is the same across both resistors.

$$V_2 = V_3 = 1.81 \text{ V}$$

$$I_{R2} = \frac{1.81}{40} = 0.045 \text{ A}$$

$$I_{R3} = \frac{1.81}{20} = 0.091 \text{ A}$$

---

---

---

---

---

---

---

---

## Power

- Electric power is the rate at which electric energy is transferred in a circuit.

$$P = IV$$

- The power could be converted to mechanical energy, for example in a motor.
- The power could also be dissipated as heat from the resistance in the circuit.

---

---

---

---

---

---

---

---

- We can use Ohm's law to substitute for either voltage or current.

$$P = I^2R$$

$$P = \frac{V^2}{R}$$

---

---

---

---

---

---

---

---