

Chapter 19

① A    ② B    ③ B    ④ D    ⑤ A

⑦ A    ⑧ B

⑨ A     $P = \frac{V^2}{R}$     ⑩ B     $P = \frac{I^2 R}{(2I)^2 R}$

⑪ D     $I = \frac{q}{t}$     In one second  
 $q = 2(1.6 \times 10^{-19})(2 \times 10^6)(10^8)$

$$I = \frac{2(1.6 \times 10^{-19})(2 \times 10^6) 10^8}{1} = 6.4 \times 10^{-5} A$$

⑫ A

⑬ A    option A:  $I = \frac{V}{R} = \frac{5+9}{30+50} = \frac{14}{80} = 0.175$

option B:  $I = \frac{V}{R} = \frac{5+12}{10+20+40} = \frac{17}{70} = 0.243$

option C:  $I = \frac{V}{R} = \frac{5+9+12}{10+20+30} = \frac{26}{60} = 0.433$

⑭ B     $100 + 40 = 140 \Omega$

⑯ A

(17) A

The three resistors are in parallel.

$$\frac{1}{R_{eq}} = \frac{1}{75} + \frac{1}{20} + \frac{1}{100} = 0.7333$$

$$R_{eq} = 13.64 \Omega$$

(18) D

(a) In parallel, the voltage drop across both is the same.

$P = \frac{V^2}{R}$  therefore, the lamp with the smaller resistance will dissipate more power (brighter)

(b) In series, the current is the same through both.

$P = I^2 R$  therefore, the lamp with the greater resistance will dissipate more power (brighter)

(19) D

$$P_{on} - P_{off} = P_{screen}$$

$$I_{on}V - I_{off}V = P_{screen}$$

$$(0.9 - 0.4)16 = P_{screen}$$



8W

(20) B

$$I = \frac{q}{t} \quad V = IR$$


$$V = \frac{qR}{t} = \frac{(6)(100)}{60} = 10V$$

(22) D

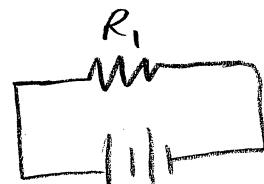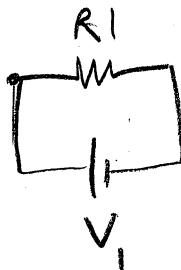

$$V = V_1 + 9$$

$$I = 0.3A$$

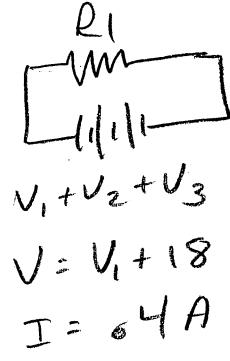

$$V = V_1 + 18$$

$$I = 0.4A$$

$$V = IR$$

$$V_1 + 9 = 0.3R_1 \quad V_1 + 18 = 0.4R_1$$

$$V_1 = 0.3R_1 - 9 \quad V_1 = 0.4R_1 - 18$$

$$0.3R_1 - 9 = 0.4R_1 - 18$$

$$9 = 0.1R_1$$

$$R_1 = 90\Omega$$

(23) B

$$R_{eq} = (8\Omega) \times 2 = 16\Omega$$

$$V = IR = 0.15(160) = 24V$$

(24) C



$$I_{30} = \frac{V_{30}}{R_{30}} = \frac{4.5}{30} = 0.15A$$

$$I_{50} = I_{30} \text{ series.}$$

$$V_{50} = I_{50} R_{50} = (0.15)(50) = 7.5V$$


$$V_{battery} = V_{30} + V_{50} = 4.5 + 7.5 = 12V$$

(25) B

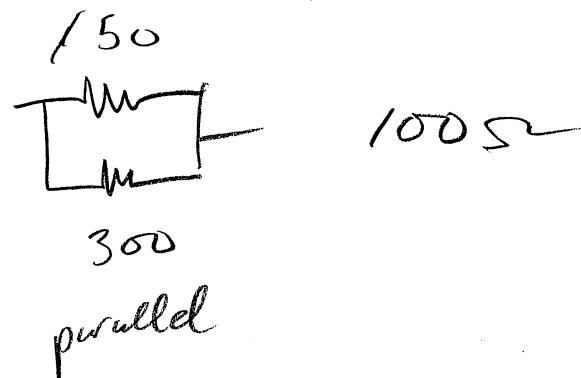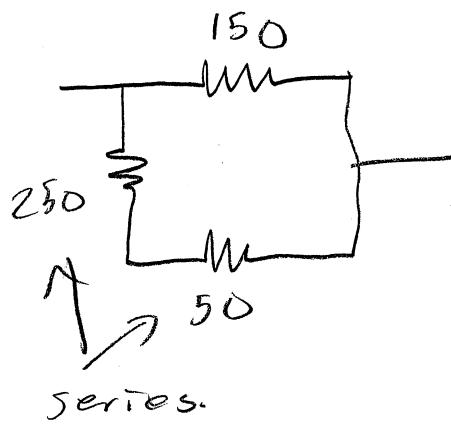


series.


(26) A

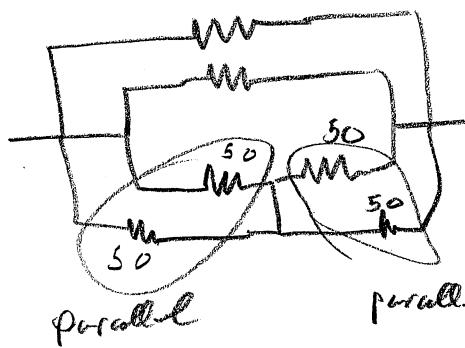

parallel      parallel

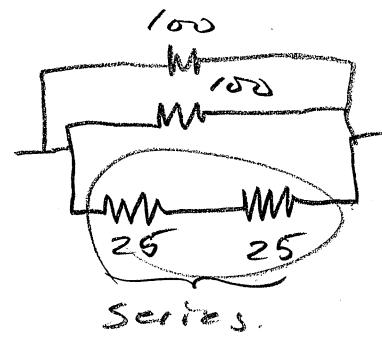

series.

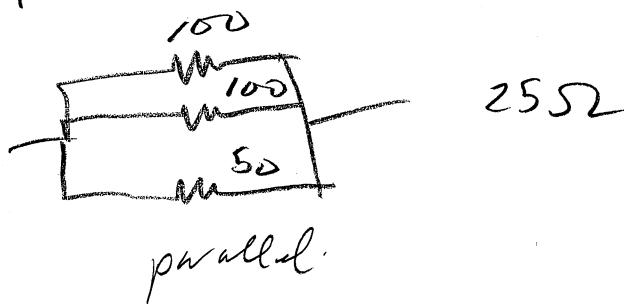

parallel.

(27) B

$$P = IV$$

$$I = \frac{P}{V} = \frac{120}{12} = 10 \text{ A}$$

(33) D

$$V = IR_1, \quad V = 2IR_2$$

$$R_1 = \frac{V}{I} \quad R_2 = \frac{V}{2I}$$

$$\frac{R_1}{R_2} = \frac{\frac{V}{I}}{\frac{V}{2I}} = 2$$

(35) B

(37) A

$$V = IR$$

$$I = \frac{V}{R} = \frac{10}{100} = 0.1$$

(38) D

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{80R}{8} = \frac{80R}{10} + \frac{80R}{R}$$

$$10R = 8R + 80$$

$$2R = 80$$

$$R = 40 \Omega$$

(39) C

(40) B

(41) A

$$P = IV$$

$$= (0.12)(3) = 0.36W$$

(42) A

(43) B


$$V = IR$$

$$I = \frac{V}{R} = \frac{12}{100} = 0.12$$

(44) C

$$R = \frac{V}{I} = \frac{9}{0.15} = 60 \Omega$$

(45) A

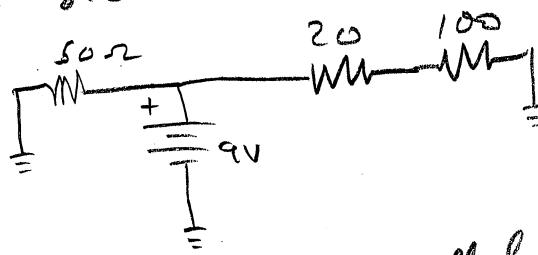

Branches are parallel, voltage drop across each is the same.

$$V = IR$$

$$I = \frac{V}{R} = \frac{9}{120}$$

(51) B

(52) B

$$V=IR$$

$$I = \frac{V}{R} = \frac{9}{75} = 0.12 \text{ A}$$

(53) C

$$V=IR$$

$$R = \frac{V}{I} = \frac{9}{0.25} = 36 \Omega$$

(54) C

(55) B

in parallel - increasing one resistor increases the equivalent resistance.

$V=IR$  increased  $R$ , decreases  $I$   
(constant voltage)

(56) B

(57) B

increasing current with constant resistance increases power.  
( $P = I^2 R$ )

increasing resistance with constant voltage decreases power ( $P = \frac{V^2}{R}$ )

(58) C

reducing voltage with constant resistance decreases power ( $P = \frac{V^2}{R}$ )

decreasing resistance with constant current decreases power ( $P = I^2 R$ )

(59) C

$$P = \frac{V^2}{R} = \frac{(9)^2}{(3 \times 10)} = 2.7$$

(61) A

(62) B

(63) D

(65) A

resistors are in parallel so  
voltage is the same across all  
resistors.

$$I_1 = \frac{V}{R_1} = \frac{24}{50} = 0.48A \quad I_2 = \frac{V}{R_2} = \frac{24}{80} = 0.3A$$

$$I_3 = \frac{V}{R_3} = \frac{24}{20} = 1.2A \quad I_4 = \frac{V}{R_4} = \frac{24}{100} = 0.24A$$

(66) B

(67) C

Adding a second resistor increases  
the total resistance.

The voltage remains the same.

$P = \frac{V^2}{R}$ , so power decreases.