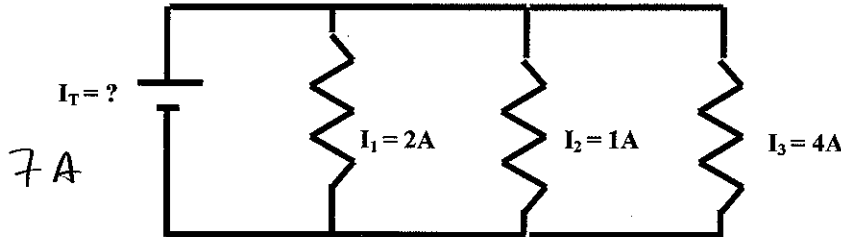



CIRCUIT MATH

Solve the following problems showing all work.

1. Find I_T for the following circuit.




2. Complete the table for this circuit.

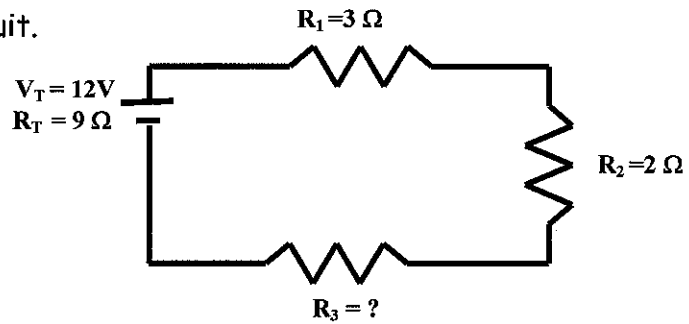


$V_T = 12 \text{ V}$	$V_1 = 3.9 \text{ V}$	$V_2 = 2.6 \text{ V}$	$V_3 = 5.2 \text{ V}$
$R_T = 9 \Omega$	$R_1 = 3 \Omega$	$R_2 = 2 \Omega$	$R_3 = 4 \Omega$
$I_T = 1.3 \text{ A}$	$I_1 = 1.3 \text{ A}$	$I_2 = 1.3 \text{ A}$	$I_3 = 1.3 \text{ A}$

3. Complete the table for this circuit.

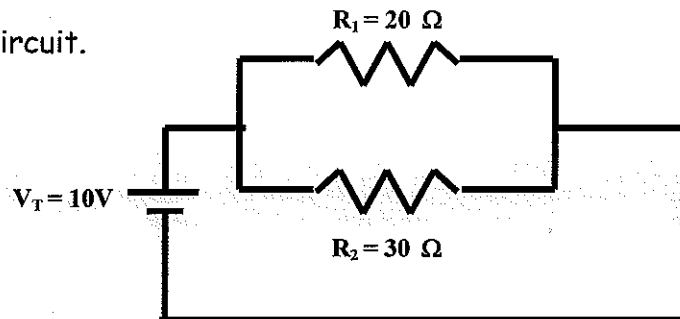

$V_T = 10 \text{ V}$	$V_1 = 10 \text{ V}$	$V_2 = 10 \text{ V}$
$R_T = 12 \Omega$	$R_1 = 20 \Omega$	$R_2 = 30 \Omega$
$I_T = 0.83$	$I_1 = 0.5 \text{ A}$	$I_2 = 0.33 \text{ A}$

4. Find the following.

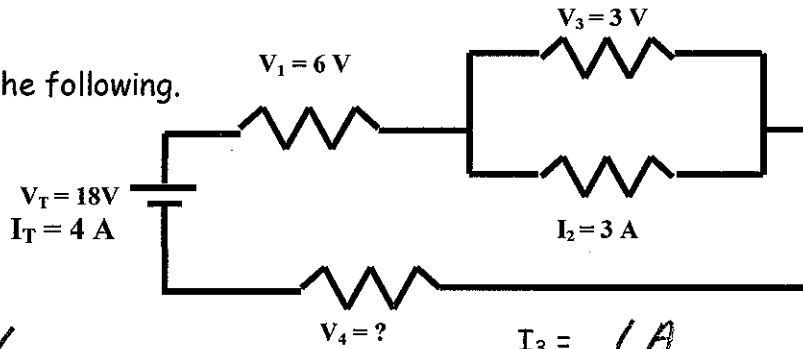


$V_2 = \underline{3V}$

$I_3 = \underline{1A}$

$V_4 = \underline{9V}$

$I_4 = \underline{4A}$

5. Find the following.

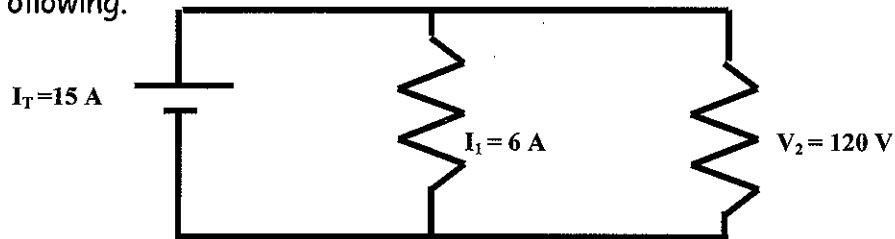

$V_T = \underline{120V}$


$R_1 = \underline{20\Omega}$

$V_1 = \underline{120V}$

$R_2 = \underline{13.3\Omega}$

$I_2 = \underline{9A}$

6. Find the following.

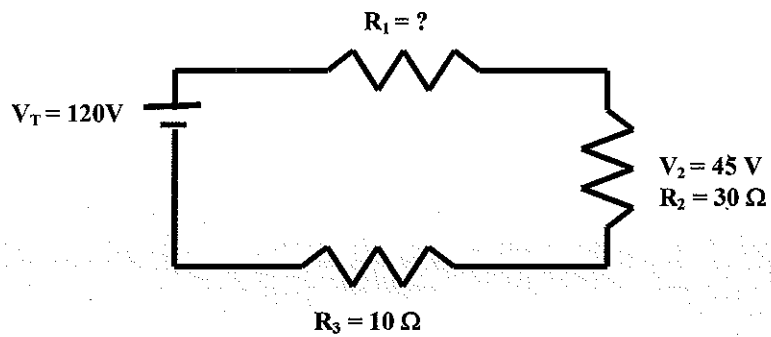

$V_3 = \underline{15V}$

$I_3 = \underline{1.5A}$

$V_1 = \underline{60V}$


$R_1 = \underline{40\Omega}$

$I_1 = \underline{1.5A}$

$R_T = \underline{80\Omega}$

$I_2 = \underline{1.5A}$

7. Find the following.

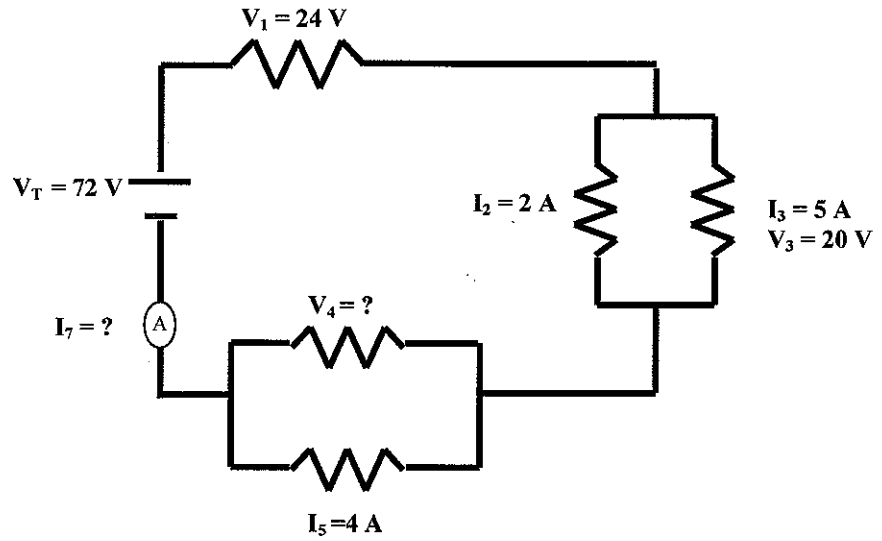

$$I_1 = \underline{7A}$$

$$V_2 = \underline{20V}$$

$$V_4 = \underline{28V}$$

$$V_5 = \underline{28V}$$

$$I_4 = \underline{3A}$$

$$I_7 = \underline{7A}$$