
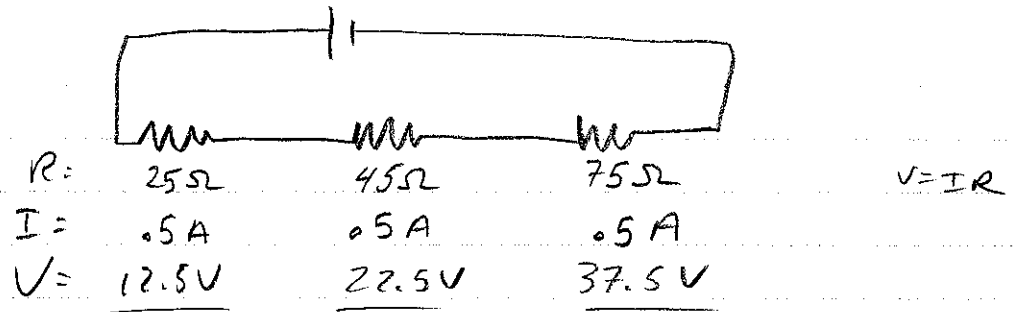


Circuits Worksheet

①

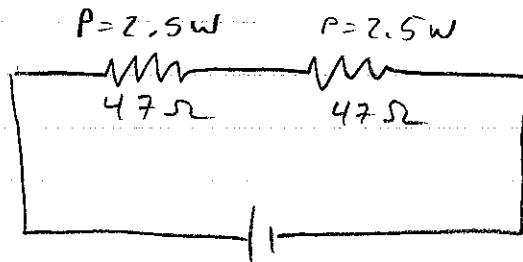

②



$$R_T = 47 + 47 = 94\Omega$$


$$P_T = 2.5 + 2.5 = 5W$$

$$P = \frac{V^2}{R}$$

$$5 = \frac{V^2}{94}$$

$$V = \underline{21.7V}$$

③

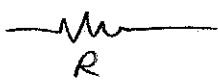

$$I = 15A$$



$$I = 12A$$

The voltage would be the same for both circuits
(we are adding to 8Ω resistor)

$$V = IR$$

$$15(R) = 12(R + 8)$$

$$15R = 12R + 96$$

$$3R = 96$$

$$R = \underline{32\Omega}$$

④

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{115} = \frac{1}{155} + \frac{1}{R_2}$$

$$.002244 = \frac{1}{R_2}$$

$$R_2 = \underline{446 \Omega}$$

⑤


$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

$$\frac{1}{R_p} = N \left(\frac{1}{R} \right)$$

$$.063 = N \left(\frac{1}{4} \right)$$

$$N = 64 \quad (\text{we must round up to the nearest whole number, you can't have a fraction of a resistor})$$

⑥

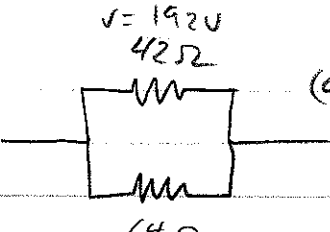

(a) $I = 4.6 \text{ A}$

(b) Total $I = 3 + 4.6 = 7.6 \text{ A}$


$$P = IV$$

$$= (7.6)(192)$$

$$= \underline{1459 \text{ W}}$$

$I = 3 \text{ A}$
 $V = 192 \text{ V}$

⑦

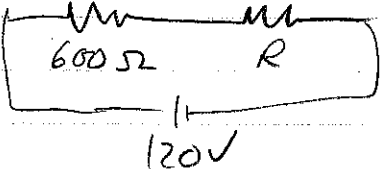






$$P = \frac{V^2}{R}$$

$$18 = \frac{(120)^2}{(600 + R)}$$



$$18(600 + R) = 14400$$



$$10800 + 18R = 14400$$

$$R = \underline{200 \Omega}$$

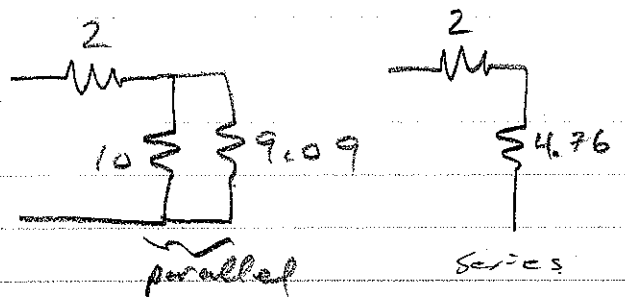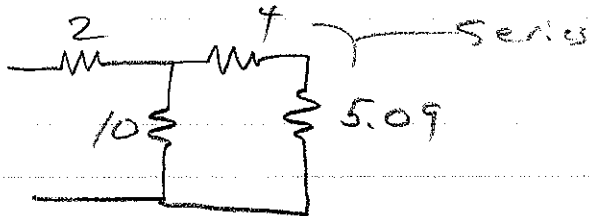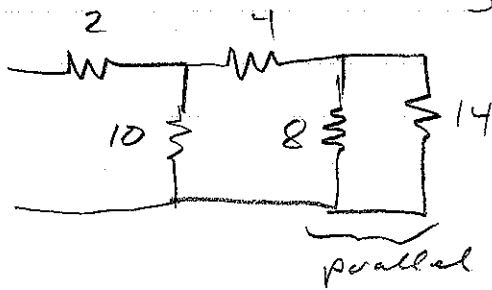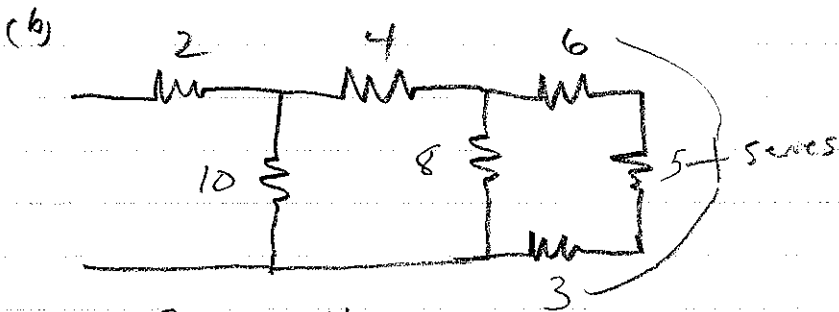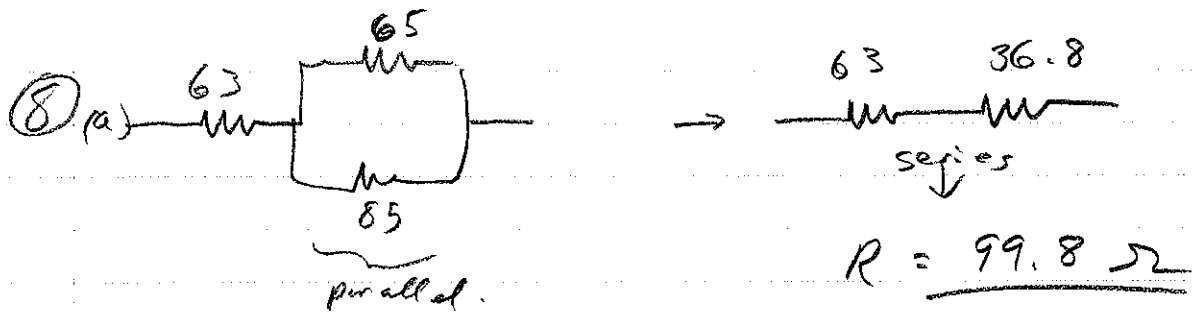

$R = 6.76$

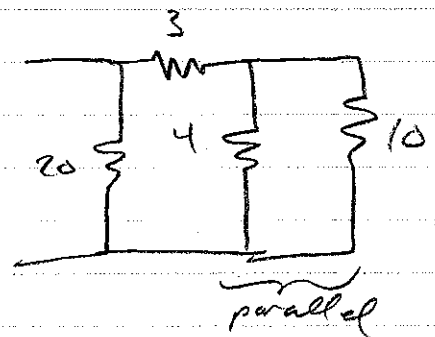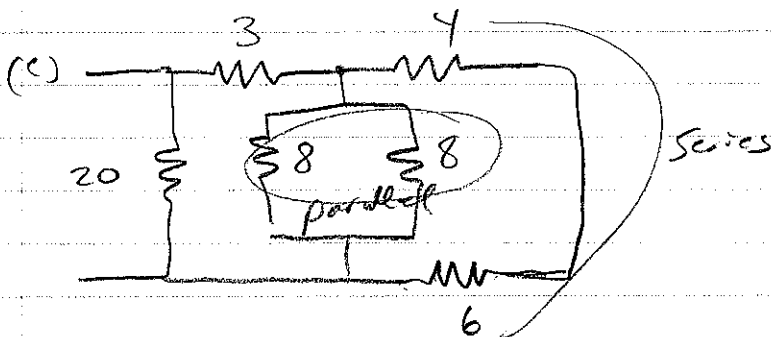

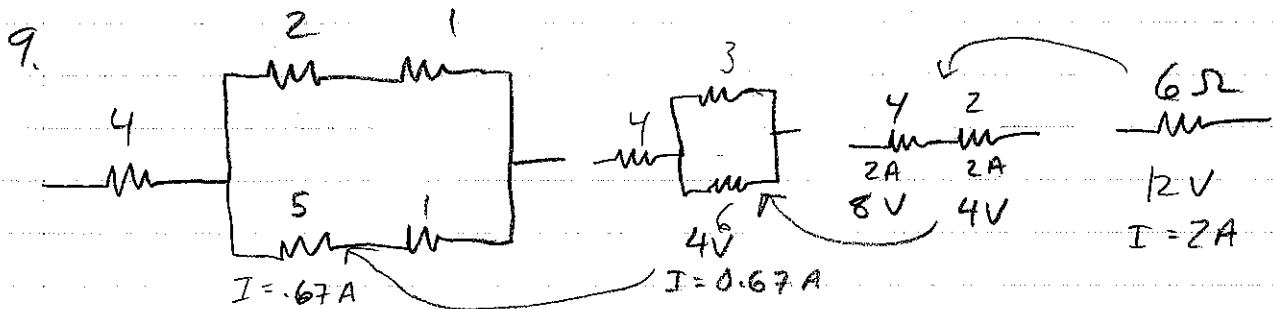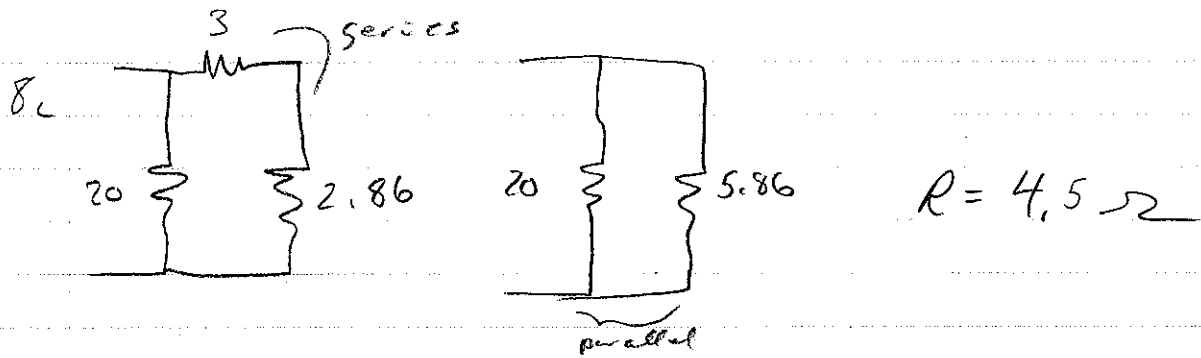

$$P = I^2 R = (0.67)^2 5 = \underline{2.2 W}$$

$$\textcircled{10} V_8 = 0.5(8) = 4V$$

$$\text{So } V_{16} = 4V + I_{16} = \frac{4}{16} = 0.25A$$

$$\text{current through } 20\Omega = 0.5A + 0.25A = 0.75A$$

$$V_{20} = (0.75)(20) = 15V$$

$$V_{9\Omega} + V_{19\Omega} = V_{20\Omega} + 4V = 19V$$

$$\text{So } I_{9\Omega} = \frac{19}{9} = \underline{2.11 V}$$