
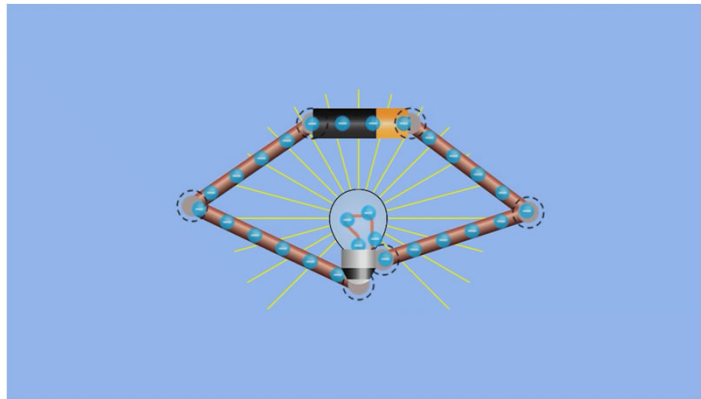


Electric Current

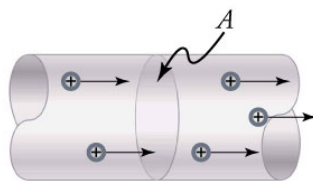- An electric current occurs when charges move through a wire.



- Current is defined as the rate at which charge flows through a circuit.



Physics. OpenStax. <https://openstax.org/books/physics/pages/19-1-ohms-law> (CC BY 4.0)

$$I = \frac{Q}{t}$$

Where:

Q – charge (coulomb, C)

t – time (seconds, s)

I – current (amperes, amps, A)

Example 1

- A total charge of 5 nC move past an area in a time 1 ns. Calculate the current in the wire.

$$I = \frac{Q}{t}$$
$$I = \frac{5 \times 10^{-9} \text{ C}}{1 \times 10^{-9} \text{ s}}$$
$$I = 5 \text{ A}$$

Example 2

- A lightning strike can transfer as many as 10^{20} electrons from the cloud to the ground. If the strike lasts 2 ms, what is the average electric current in the lightning?

$$I = \frac{Q}{t}$$
$$Q = (10^{20})(1.6 \times 10^{-19}) = 16 \text{ C}$$
$$I = \frac{16 \text{ C}}{2 \times 10^{-3} \text{ s}}$$
$$I = 8000 \text{ A}$$

Electric Potential

- Electric potential is the electric potential energy per unit charge.

$$V = \frac{E}{Q}$$

Where:

E – electric potential energy (joules, J)

Q – charge (coulombs, C)

V – electric potential, voltage (volts, V)

Example

- An electron is exposed to an electric potential of 200 V. Calculate the potential energy.

$$V = \frac{E}{Q}$$

$$200 = \frac{E}{1.6 \times 10^{-19}}$$

$$E = 3.2 \times 10^{-17} \text{ J}$$

Current vs Voltage

- Current is related to the number of charges.
- Voltage (potential) is related to the energy of each charge.

Resistance

- The motion of charges in a wire can be affected by many factors, including impurities in the metal of the wire or collisions between other charges in the material.
- This is called **resistance**.
- Every time a collision occurs, some of the energy is transformed into heat.

- Georg Ohm (German), 1827
 - current through a conductor is proportional to the voltage drop across a current-carrying conductor

$$V = IR$$



Georg Ohm – Unknown (public domain)

Where:


I – current (amperes, amps, A)

R – resistance (ohms, Ω)

V – voltage drop (volts, V)

Privacy & Terms

V = I R

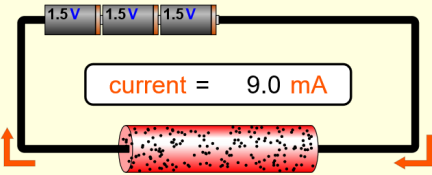

current = 9.0 mA

V
voltage



R
resistance

4.5 V 500 Ω


Ohm's Law

PIET


Schematic Symbols

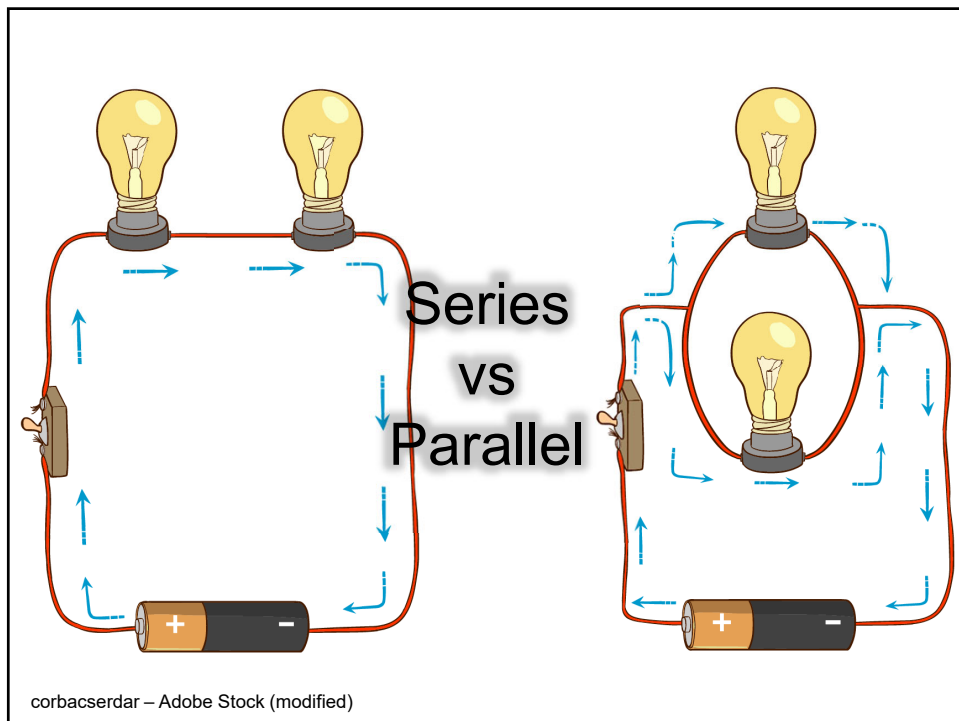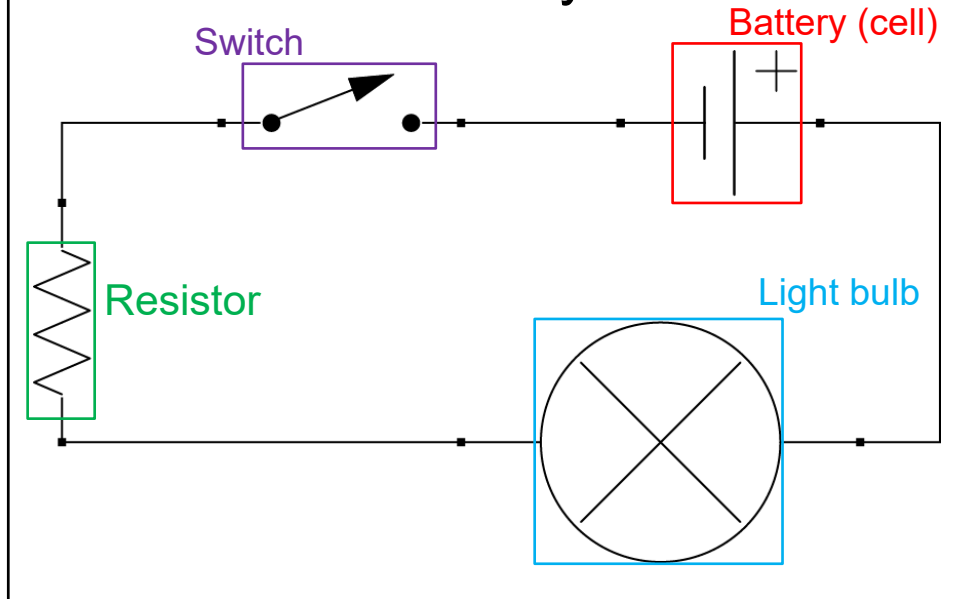


SERIES AND PARALLEL CIRCUITS

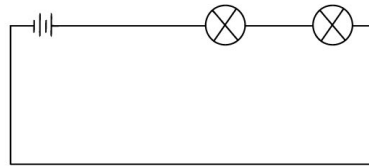


Series Circuit

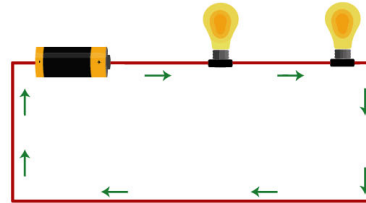

Series Circuit

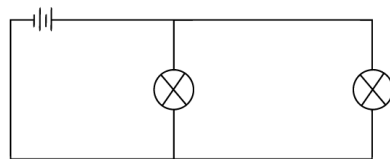


Parallel Circuit

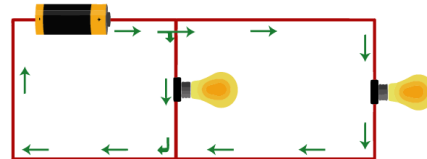

Parallel Circuit


Series

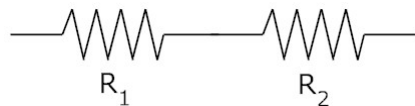
- Current flows directly from one component to the next



Parallel

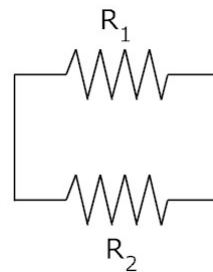- Current splits and part of it passes through each component



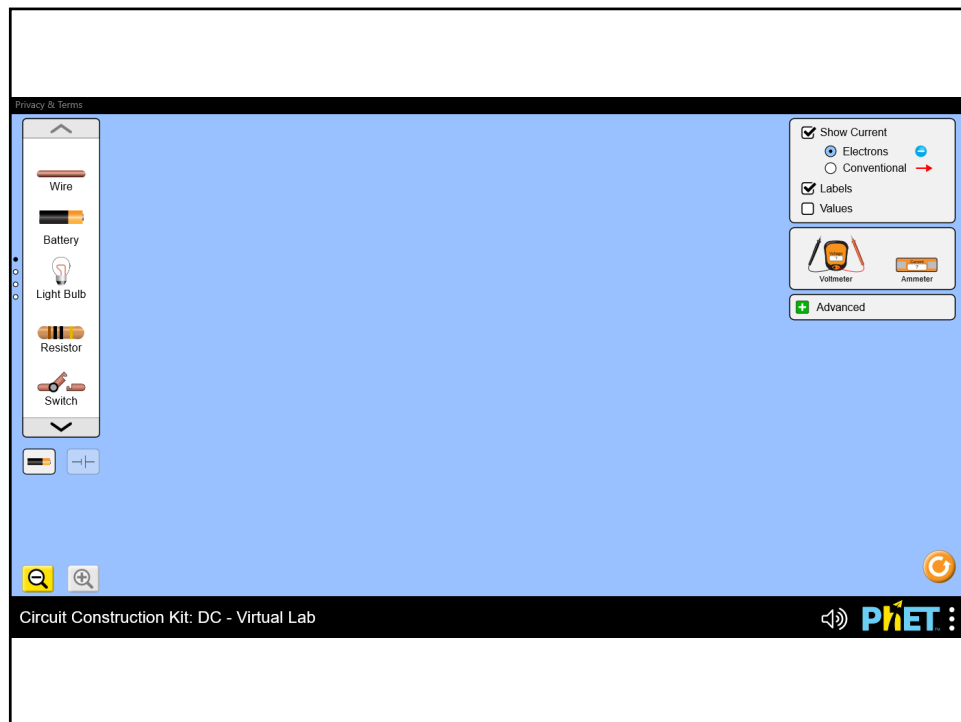

Series

- **Current** is the **same** through all the components
- **Adding resistors** (components) without changing voltage **decreases total current** in the circuit

Parallel

- **Voltage** drop is the **same** across all components
- **Adding resistors** (components) without changing voltage **increases total current** in the circuit

Series

- **Adding** resistors (components) **increases** total resistance


Parallel

- **Adding** resistors (components) **decreases** total resistance

Batteries (Cells)


Series

- **Voltage** adds

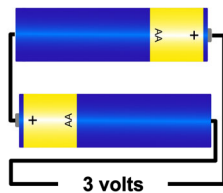


Parallel

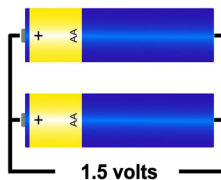- **Voltage** is the **same**
- Increases Amp hour capacity
- the amount of time the battery can deliver an amount of energy (voltage)



Charles Risen (Adobe Stock)

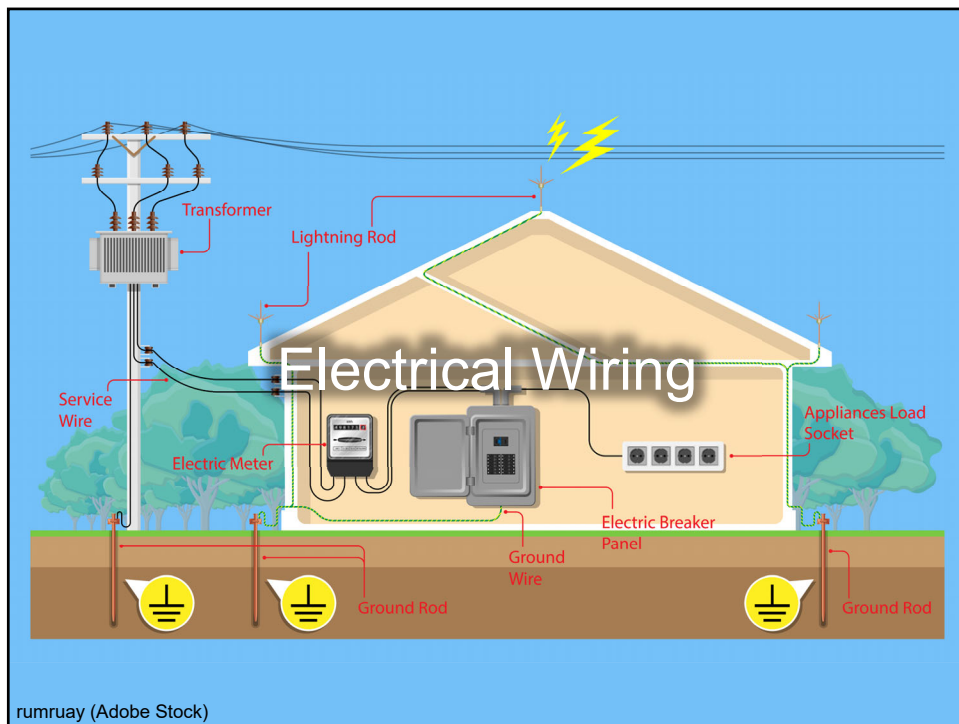


- Buildings are wired in parallel.
 - Voltage is the same for all appliances.
 - Consistent voltage everywhere throughout the country.
 - Appliances will work anywhere.
 - Each appliance added to the circuit increases the current in the circuit.
 - More charges flowing through the wire increases the number of collisions which increases rate of energy transformation to heat possibly resulting in a fire.




Thicha (Adobe Stock)

Safety

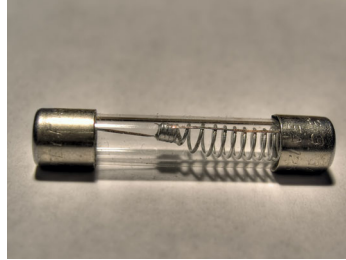- Fuse
 - Limits the amount of current flowing in the circuit.
 - A thin wire in a sealed glass container.
 - Heat generated by resistance increases with current until the wire melts thus breaking the circuit.



Fuse – Razor512 ([CC BY 2.0](#))

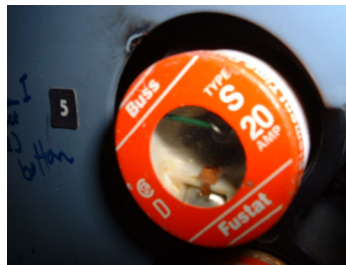


Fuse – David Loomer ([CC BY-NC-ND 2.0](#))


- Circuit breaker
 - Limits the amount of current flowing in the circuit.
 - A switch and an electromagnet attached to the circuit.
 - The electromagnet gets stronger as the current increases until it attracts a metal lever on the switch causing it to turn off.



Lost_in_the_Midwest (Adobe Stock)

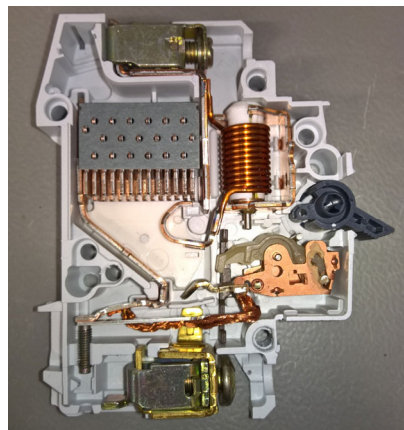

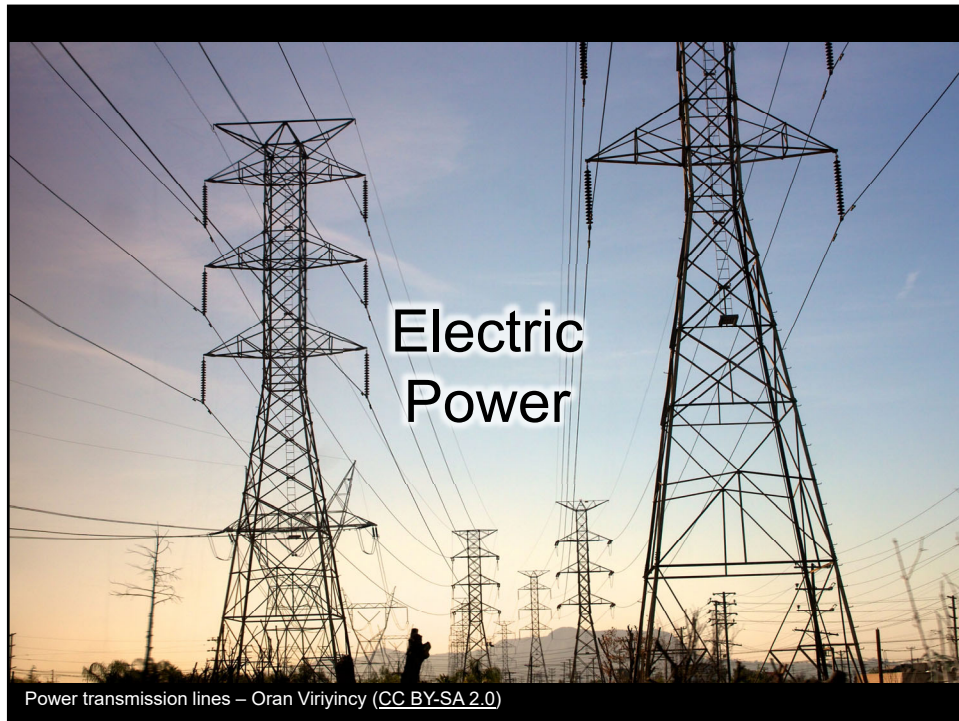Circuit breaker – jarvelajussi ([CC BY-NC 2.0](#))



Power

- Rate at which energy is transferred.

$$P = \frac{E}{t}$$

P – power (watts, W)

E – energy (joules, J)

t – time (seconds, s)

- In an electric circuit, power can be related to current and voltage.

$$P = IV$$

P – power (watts, W)

I – current (amperes, A)

V – potential (voltage, V)

Example

- A 60 W light bulb dissipates (uses) 60 W of power. The voltage drop across the light bulb is 120 V.
 - a) Calculate the current flowing through the bulb.
 - b) How much energy does the bulb use in one hour?

a) current flowing through the bulb

$$P = IV$$

$$I = \frac{P}{V}$$

$$I = \frac{60 \text{ W}}{120 \text{ V}} = 0.5 \text{ A}$$

b) energy the bulb uses in one hour

$$P = \frac{E}{t}$$

$$E = Pt$$

$$E = 60 \text{ W}(1 \times 60 \times 60)\text{s} = 216000 \text{ J}$$

Cost of Electricity

- Electrical devices use power.
 - The amount of power depends on current (and voltage).
- The amount of energy used depends on the amount of time the device operates.
- A 60W light bulb uses 60 Watts of power or 60 Joules of energy each second.
 - In one minute (60 s), it will use 360 J.
 - In one hour (3600 s), it will use 216000 J.

- Power companies charge for the energy used.
- Using Joules as the units for energy would mean the numbers would be very large.
- A different unit of energy, kWh (kilowatt hour), was developed so that the energy numbers would be more manageable.

$$1 \text{ kWh} = 1000 \times 3600 = 3.6 \times 10^6 \text{ J}$$


- Appliances often list how much power they use (in Watts, W)



- To calculate the amount of energy used (in kWh) in one hour

$$\frac{\text{Power (W)}}{1000} \times \text{time (hours)}$$

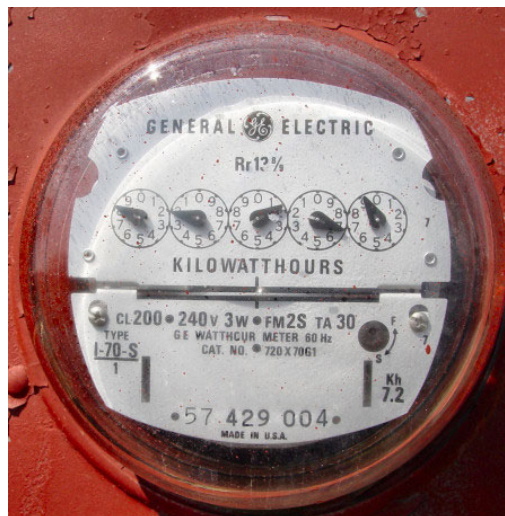- A power meter measures the amount of energy used.



Red Power - Scott Robinson (CC BY 2.0)

Example 1

A household uses 900 kWh in one month. The cost of electricity is 9 ¢/kWh. Calculate the total cost for the month.

$$\text{Cost} = 900 \text{ kWh} \times \$0.09$$

$$\text{Cost} = \$81$$

Example 2


A computer uses 385 W of power. What is the cost of letting the computer run all day if electricity is \$0.09/kWh?

$$\text{Cost} = \frac{385 \text{ W}}{1000} \times 24 \text{ h} \times \$0.09$$

$$\text{Cost} = \$0.83$$

Where does the electricity that powers our lives come from?


Electric Power Distribution

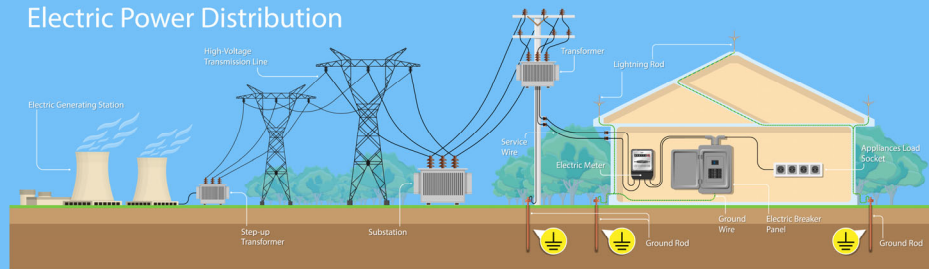

rumruay (Adobe Stock)

Mechanical

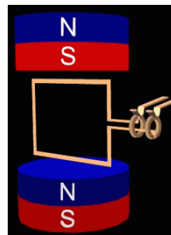- A generator uses electromagnetic induction to produce electricity.
 - A coil spinning in a magnetic field.



from [PHYSCLIPS](#)

- The generator is either driven directly or through a secondary process.

- Hydroelectric
 - Water directly drives the generator.
- Coal/Gas/Oil
 - Fuel is burned to boil water creating steam to drive the generator.
- Nuclear
 - Heat from a nuclear fission reaction used to boil water creating steam to drive the generator.




Manitoba Hydro Pointe du Bois Generator – Wtshymanki (Public Domain)



Hoover Dam generators – Jon Sullivan (Public Domain)

Chemical

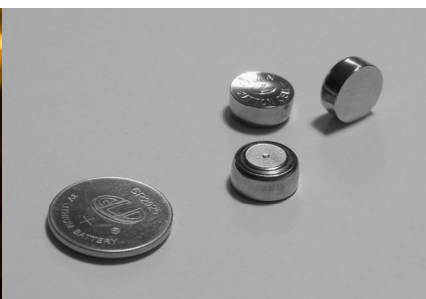- The moving electrons from a redox reaction can be harnessed to do work.
 - battery



Batteries at Attention – massmatt ([CC BY 2.0](#))
Batteries – James Bowe ([CC BY 2.0](#))

Light

- Photovoltaic cells absorb light energy, usually from the sun, and transfer it to electrons allowing them to flow creating an electrical current.



Solar Panel for Solar Highway – Portland General Electric ([CC BY-ND 2.0](#))


**Devices that Work by
Generating Small Amounts of
Electricity**

A collage of four images arranged in a 2x2 grid. The top-left image shows a white digital thermometer with two displays: 'OUT 32.4°C' and 'IN 23.6°C'. The top-right image shows a silver wristwatch with a blue dial and a grey mesh strap. The bottom-left image shows a vintage-style microphone with a gold grille. The bottom-right image shows a round Nest Learning Thermostat with a black face and an orange display showing '21'.

snc10614 – Par Johansson ([CC BY-SA 2.0](#))
Hamilton Khaki – James Case ([CC BY 2.0](#))
Microphone – ngad (Adobe Stock)
Nest Learning Thermostat showing Celsius – Nest ([CC BY-NC-ND 2.0](#))

Thermocouple

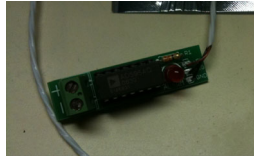- Two wire legs made from different metals welded together at one end, creating a junction.
 - When the junction experiences a change in temperature, a voltage is created.
 - Used to measure temperature.



MakerBot Thermocouple Sensor – Andrew Plumb ([CC BY-SA 2.0](#))
Easy To Read-Easy To Install – Jo Zimny Photos ([CC BY-NC-ND 2.0](#))

Piezoelectricity

- The appearance of an electrical potential (voltage) across the sides of a crystal when you subject it to mechanical stress (by squeezing it).
 - microphone, quartz watch



Microphone – mipan (Adobe Stock)
Quartz Movement – Julie Jablonski ([CC BY-NC 2.0](#))